Giao Tran

Convert 1-bit ALU to 4-bit ALU and change ALU module instantiation in ALU top module from explicit name port connection to dot-star port connection

Alu_top code

```
// N-bit ALU behavioral code
     timescale 1ns/1ps
    module alu_top // Module start declaration
    #(parameter N=4) // Parameter declaration
5 ₽( input logic clk, reset,
       input logic[N-1:0]operand1, operand2,
       input logic[1:0] operation,
      output logic[N-1:0] result
8
9 ();
      // Local net declaration
     logic[N-1:0] alu out;
     // Instantiation of module alu
14
15 p alu #(.N(N)) alu instance(
     .opnd1 (operand1),
16
        .opnd2(operand2),
        .operation(operation),
        .out (alu out)
      defparam alu instance.N=4;
24
      // Register alu output
25 palways@(posedge clk or posedge reset) begin
       if(reset == 1) begin
26 🛊
         result <= 0;
        end
29 自
        else begin
         result <= alu out;
      end
33 endmodule: alu top // Module alu top end declaration
```


alu code:

```
// 1-bit ALU behavioral code
     `timescale 1ns/1ps
    module alu // Module start declaration
    #(parameter N=1) // Parameter declaration
 5
  □ (
 6
      input logic[N-1:0] opnd1, opnd2,
7
      input logic[1:0] operation,
8
      output logic[N-1:0] out
9
   L);
10
      always@(opnd1 or opnd2 or operation)
11 □
      begin
12
        case (operation)
13
          2'b00: out = opnd1 + opnd2;
14
          2'b01: out = opnd1 - opnd2;
15
          2'b10: out = opnd1 & opnd2;
16
          2'b11: out = opnd1 | opnd2;
17
        endcase
18
      end
19
    endmodule: alu
```


Testbench code:

```
1 //1-bit ALU testbench code
       `timescale 1ns/1ps
      module alu_top_testbench;
      parameter \overline{N} = \overline{4};
      logic clock, reset;
     logic [N-1:0] operand1, operand2;
      logic [N-1:0] result;
     logic [1:0] operation;
 10 // Instantiate design under test
 11 ⊟alu top #(.N(N)) design instance(
     .clk(clock),
     .reset(reset),
 14
       .operand1 (operand1),
      .operand2(operand2),
 16
     .operation(operation),
       .result (result)
 18 );
 19
 20 pinitial begin
 21 // Initialize Inputs
      reset = 1;
     clock = 0;
 24
     operand1 = 0;
     operand2 = 0;
 26
      operation = 0;
     // Wait 20 ns for global reset to finish and start counter
 29
      #20ns;
      reset = 0;
     #20ns
      operand1 = 0;
 34
      operand2 = 1;
      operation = 0;
 36
     #20ns;
      operand1 = 1;
 39
      operand2 = 1;
 40
      operation = 1;
 41
 42
     #20ns;
 43
      operand1 = 1;
 44
      operand2 = 1;
45 operation = 2;
48 operand1 = 1;
49 operand2 = 0;
50 operation = 3;
  // Wait for 10ns
#20ns;
  // terminate simulation
$finish();
end
   // Clock generator logic
  palways@(clock) begin
    #10ns clock <= !clock;
   // Print input and output signals
  ≡initial begin
  $mc
    $monitor(" time=%0t, clk=%b reset=%b operation=%d, operand1=%d, operand2=%d", $time, clock, reset, operation, operand1);
68 endmodule
```


a. 1 bit alu RTL

 

b. 1 bit alu Post mapping

 

c. 1 bit alu Post fitting

 

d. 1 bit alu Resource usage summary


| | Resource | Usage |
|----|--|----------------|
| 1 | Estimated ALUTs Used | 1 |
| 1 | Combinational ALUTs | 1 |
| 2 | Memory ALUTs | 0 |
| 3 | LUT_REGs | 0 |
| 2 | Dedicated logic registers | 1 |
| 3 | | |
| 4 | Estimated ALUTs Unavailable | 0 |
| 1 | Due to unpartnered combinational logic | 0 |
| 2 | Due to Memory ALUTs | 0 |
| 5 | | |
| 6 | Total combinational functions | 1 |
| 7 | Combinational ALUT usage by number of inputs | |
| 1 | 7 input functions | 0 |
| 2 | 6 input functions | 0 |
| 3 | 5 input functions | 0 |
| 4 | 4 input functions | 1 |
| 5 | <=3 input functions | 0 |
| 8 | | |
| 9 | Combinational ALUTs by mode | |
| 1 | normal mode | 1 |
| 2 | extended LUT mode | 0 |
| 3 | arithmetic mode | 0 |
| 4 | shared arithmetic mode | 0 |
| 10 | | |
| 11 | Estimated ALUT/register pairs used | 1 |
| 12 | | |
| 13 | Total registers | 1 |
| 1 | Dedicated logic registers | 1 |
| 2 | I/O registers | 0 |
| 3 | LUT_REGs | 0 |
| 14 | | |
| 15 | | |
| 16 | I/O pins | 7 |
| 17 | | |
| 18 | DSP block 18-bit elements | 0 |
| 19 | | |
| 20 | Maximum fan-out node | result[0]~reg0 |
| 21 | Maximum fan-out | 1 |
| 22 | Total fan-out | 15 |
| 23 | Average fan-out | 0.94 |

Number of ALUT: 1 (7 I/O pins)

Normal mode: 1

Number of Functions: 1 (4 input function)

 e. 1 bit alu Waveform simulation and transcript



```
Transcript :
# Errors: 0, Warnings: 0
# vsim work.alu_top_testbench
# Start time: 16:14:52 on Jan 26,2021
# Loading sv_std.std
# Loading work.alu_top_testbench
# Loading work.alu_top
# Loading work.alu
add wave -position insertpoint sim:/alu_top_testbench/*
VSIM 10> run -all
  time=0, clk=0 reset=1 operation=0, operand1=0, operand2=0
  time=10000, clk=1 reset=1 operation=0, operand1=0, operand2=0
  time=20000, clk=0 reset=0 operation=0, operand1=0, operand2=0
  time=30000, clk=1 reset=0 operation=0, operand1=0, operand2=0
  time=40000, clk=0 reset=0 operation=0, operand1=0, operand2=1
  time=50000, clk=1 reset=0 operation=0, operand1=0, operand2=1
  time=60000, clk=0 reset=0 operation=1, operand1=1, operand2=1
   time=70000, clk=1 reset=0 operation=1, operand1=1, operand2=1
  time=80000, clk=0 reset=0 operation=2, operandl=1, operand2=1
  time=90000, clk=1 reset=0 operation=2, operand1=1, operand2=1
  time=100000, clk=0 reset=0 operation=3, operand1=1, operand2=0
  time=110000, clk=1 reset=0 operation=3, operand1=1, operand2=0
                    : C:/Users/user/Desktop/ECE 111 HW/Lab2/Lab2/alu_top/alu_top_testbench.sv(56)
  ** Note: $finish
     Time: 120 ns Iteration: 0 Instance: /alu_top_testbench
# Break in Module alu_top_testbench at C:/Users/user/Desktop/ECE 111 HW/Lab2/Lab2/alu_top/alu_top_testbench.sv line 56
```

Converting explicit name port connection to dot-star port connection

```
// N-bit ALU behavioral code
    `timescale 1ns/1ps
   module alu_top // Module start declaration
   #(parameter N=1) // Parameter declaration
5 □ ( input logic clk, reset,
       input logic[N-1:0] opnd1, opnd2,
       input logic[1:0] operation,
8
       output logic[N-1:0] result
9 L);
      // Local net declaration
     logic[N-1:0] out;
14
      // Instantiation of module alu
      alu #(.N(N)) alu_instance(.*);
16
      // Register alu output
18 = always@(posedge clk or posedge reset) begin
19 🛓
       if(reset == 1) begin
        result <= 0;
        end
        else begin
        result <= out;
2.4
        end
    endmodule: alu_top // Module alu_top end declaration
```

We can convert to dot-star connection by matching inputs and outputs' names from the alu.sv file. Below are the changes:

- operand 1 → opnd 1
- operand 2 → opnd 2
- out_alu → out
- Anything under instantiation of a module alu is replaced by .*


Convert 1-bit ALU to 4-bit ALU

```
// N-bit ALU behavioral code
      `timescale lns/lps
module alu_top // Module start declaration
#(parameter N=4) // Parameter declaration
      ( input logic clk, reset,
        input logic[N-1:0]operand1, operand2,
input logic[1:0] operation,
           output logic[N-1:0] result
         // Local net declaration
logic[N-1:0] alu_out;
11
12
13
14
15
16
17
          // Instantiation of module alu
        alu #(.N(N)) alu instance(
           .opnd1 (operand\overline{1}),
            .opnd2(operand2),
.operation(operation),
19
20
21
22
23
24
25
26
            .out (alu_out)
          defparam alu_instance. N=4;
        /// Register alu output
always@(posedge clk or posedge reset) begin
if(reset == 1) begin
| result <= 0;
             end
               result <= alu out;
      endmodule: alu_top // Module alu_top end declaration
```


To convert 1 bit to 4 bit, change the parameter of alu_top.sv and the testbench from 1 to 4; N=4. The snapshot above is in explicit name port connection, but the code will produce the same results in dot star connection.

4 bit alu_top SystemVerilog design


a. 4 bit alu RTL

 

b. 4 bit alu Post mapping

 

c. 4 bit alu Post fitting

 

d. Resource usage summary

| | Resource | Usage |
|----|--|--------------------|
| 1 | Estimated ALUTs Used | 9 |
| 1 | Combinational ALUTs | 9 |
| 2 | Memory ALUTs | 0 |
| 3 | LUT_REGs | 0 |
| 2 | Dedicated logic registers | 4 |
| 3 | | |
| 4 | Estimated ALUTs Unavailable | 0 |
| 1 | Due to unpartnered combinational logic | 0 |
| 2 | Due to Memory ALUTs | 0 |
| 5 | | |
| 6 | Total combinational functions | 9 |
| 7 | Combinational ALUT usage by number of inputs | |
| 1 | 7 input functions | 0 |
| 2 | 6 input functions | 0 |
| 3 | 5 input functions | 0 |
| 4 | 4 input functions | 0 |
| 5 | <= 3 input functions | 9 |
| 8 | | |
| 9 | Combinational ALUTs by mode | |
| 1 | normal mode | 4 |
| 2 | extended LUT mode | 0 |
| 3 | arithmetic mode | 5 |
| 4 | shared arithmetic mode | 0 |
| 10 | | |
| 11 | Estimated ALUT/register pairs used | 9 |
| 12 | | |
| 13 | Total registers | 4 |
| 1 | Dedicated logic registers | 4 |
| 2 | I/O registers | 0 |
| 3 | LUT_REGs | 0 |
| 14 | | |
| 15 | | |
| 16 | I/O pins | 16 |
| 17 | | |
| 18 | DSP block 18-bit elements | 0 |
| 19 | | |
| 20 | Maximum fan-out node | operation[0]~input |
| 21 | Maximum fan-out | 9 |
| 22 | Total fan-out | 69 |
| 23 | Average fan-out | 1.53 |

Number of ALUT: 9 (16 I/O pins)

Normal mode: 4 Arithmetic mode: 5

Number of Functions: 9 (3 input function)

The usage table summary shows that there are nine 3 input functions even though the post map shows that 4 ALUT have 4 inputs. The reason for this is because the only operand 1, operand 2 and operation are counted as inputs why the "4th" input the carry in is not counted. The carry in is transferred from one ALUT to anothe, first enters in CIN in Adder 0~5 and exits at COUT, then enters a different ALUT. As the 9 ALUT, the 4 normal mode ALUT are used for logic applications and combinational functions such as

the AND and OR operation, while 5 arithmetic ALUT are used for addition, subtraction, and accumulation.


e. Waveform simulation and transcript




The waveform matches the expected results and operations. The 4 bit ALU decides its operation based on case commands, but this only applies when the clock is high (1). Operation 0 is addition, operation 2 is subtraction, operation 3 is AND function and operation 4 is the OR function; the results are dependent on which of these operations is performed.

Homework 2B:


a. counter_4bit RTL

 

b. counter_4bit post mapping

 

c. counter _4bit post fitting

 

d. Testbench code

```
//4-bit counder testbench code
     `timescale 1ns/1ns
module counter_4bit_testbench;
    logic clock, reset;
logic [3:0] count_value;
7 // Instantiate design under test
8 =counter_4bit #(.WIDTH(4)) design_instance(
9     .clk(clock),
10     .clear(reset),
11     .count (count
count (count_value);
14 ⊟initial begin
15 // Initialize Inputs
16 reset = 1;
    // Wait 10 ns for global reset to finish and start counter
#10;
reset = 0;
     // Wait for 200ns and reset counter
     reset=1;
     // Wait for 20ns and start counter again
    #20ns;
    reset=0;
     // Wait for 10ns
    #100ns;
// terminate simulation $finish();
36 end
38 // Clock generator logic
    Balways@(clock) begin
#10ns clock <= !clock;
end</pre>
43 // Print input and output signals
47 endmodule
```

No changes were made in the testbench


e. Resource usage summary

| | Resource | Usage |
|----|--|--------------|
| 1 | Estimated ALUTs Used | 4 |
| 1 | Combinational ALUTs | 4 |
| 2 | Memory ALUTs | 0 |
| 3 | LUT_REGs | 0 |
| 2 | Dedicated logic registers | 4 |
| 3 | | |
| 4 | Estimated ALUTs Unavailable | 0 |
| 1 | Due to unpartnered combinational logic | 0 |
| 2 | Due to Memory ALUTs | 0 |
| 5 | · | |
| 6 | Total combinational functions | 4 |
| 7 | Combinational ALUT usage by number of inputs | |
| 1 | 7 input functions | 0 |
| 2 | 6 input functions | 0 |
| 3 | 5 input functions | 0 |
| 4 | 4 input functions | 1 |
| 5 | <=3 input functions | 3 |
| 8 | · | |
| 9 | Combinational ALUTs by mode | |
| 1 | normal mode | 4 |
| 2 | extended LUT mode | 0 |
| 3 | arithmetic mode | 0 |
| 4 | shared arithmetic mode | 0 |
| 10 | | |
| 11 | Estimated ALUT/register pairs used | 4 |
| 12 | | |
| 13 | Total registers | 4 |
| 1 | Dedicated logic registers | 4 |
| 2 | I/O registers | 0 |
| 3 | LUT_REGs | 0 |
| 14 | | |
| 15 | | |
| 16 | I/O pins | 6 |
| 17 | | |
| 18 | DSP block 18-bit elements | 0 |
| 19 | | |
| 20 | Maximum fan-out node | cnt_value[0] |
| 21 | Maximum fan-out | 5 |
| 22 | Total fan-out | 32 |
| 23 | Average fan-out | 1.60 |

Number of ALUT: 4 (6 I/O pins)

Normal mode: 4
Number of Functions: 4
4 input functions: 1
=< 3 input functions: 3

f. Waveform simulation and transcript

 

Counter 4bit explanation:

The output of one counter stage is connected to the clock input of the next counter stage and the counter only counts or increments when the clock is high, which is why the same number remains the same for 20 seconds.