

N-bit Linear Feedback Shift Register (LFSR)

1. SystemVerilog RTL model

```
1  //RTL Model for Linear Feedback Shift Register
2  module lfsr
3  #(parameter N = 4) // Number of bits for LFSR, could be 2,3,4,5,6,7,8
4  (
5      input logic clk, reset, load_seed,
6      input logic[N-1:0] seed_data,
7      output logic lfsr_done,
8      output logic[N-1:0] lfsr_data
9  );
10
11  reg XOR;
12  reg [N:1]shift;
13
14  always @ (posedge clk)
15      begin
16          if(reset==1)
17              begin
18                  if(load_seed==1)
19                      shift<=seed_data;
20
21                  else if (load_seed==0)
22                      shift<={shift[N-1:1], XOR};
23              end
24          end
25
26  always @ (*)
27      begin
28          XOR=shift[N]^shift[N-1]; //the value from register N and N-1 are what being fed
29          in XOR
30          end
31
32  //alternatively I also can do what is shown below for N=2 to N=8
33  /*always @ (*) begin
34      case (N)
35          2: begin
36              XOR=shift[2]^shift[1];
37          end
38          3: begin
39              XOR=shift[3]^shift[2];
40          end
41          4: begin
42              XOR=shift[4]^shift[3];
43          end
44          5: begin
45              XOR=shift[5]^shift[4];
46          end
47          6: begin
48              XOR=shift[6]^shift[5];
49          end
50          7: begin
51              XOR=shift[7]^shift[6];
52          end
53          8: begin
54              XOR=shift[8]^shift[7];
55          end
56      endcase
57  end*/
58
59  assign lfsr_data=shift[N:1];
60  assign lfsr_done=(shift[N:1]==load_seed);
61
62  endmodule: lfsr
```

2. Resource usage table for N=4

	Resource	Usage
1	Estimated ALUTs Used	5
1	-- Combinational ALUTs	5
2	-- Memory ALUTs	0
3	-- LUT_REGS	0
2	Dedicated logic registers	4
3		
4	Estimated ALUTs Unavailable	0
1	-- Due to unpartnered combinational logic	0
2	-- Due to Memory ALUTs	0
5		
6	Total combinational functions	5
7	Combinational ALUT usage by number of inputs	
1	-- 7 input functions	0
2	-- 6 input functions	0
3	-- 5 input functions	1
4	-- 4 input functions	1
5	-- <=3 input functions	3
8		
9	Combinational ALUTs by mode	
1	-- normal mode	5
2	-- extended LUT mode	0
3	-- arithmetic mode	0
4	-- shared arithmetic mode	0
10		
11	Estimated ALUT/register pairs used	5
12		
13	Total registers	4
1	-- Dedicated logic registers	4
2	-- I/O registers	0
3	-- LUT_REGS	0
14		
15		
16	I/O pins	12
17		
18	DSP block 18-bit elements	0
19		
20	Maximum fan-out node	load_seed~input
21	Maximum fan-out	5
22	Total fan-out	47
23	Average fan-out	1.42

Number of ALUT: 5 (12 I/O pins)


Number of Functions: 5

1 5 input functions


1 4 input functions

3 3 input functions


3. RTL schematic for N=4

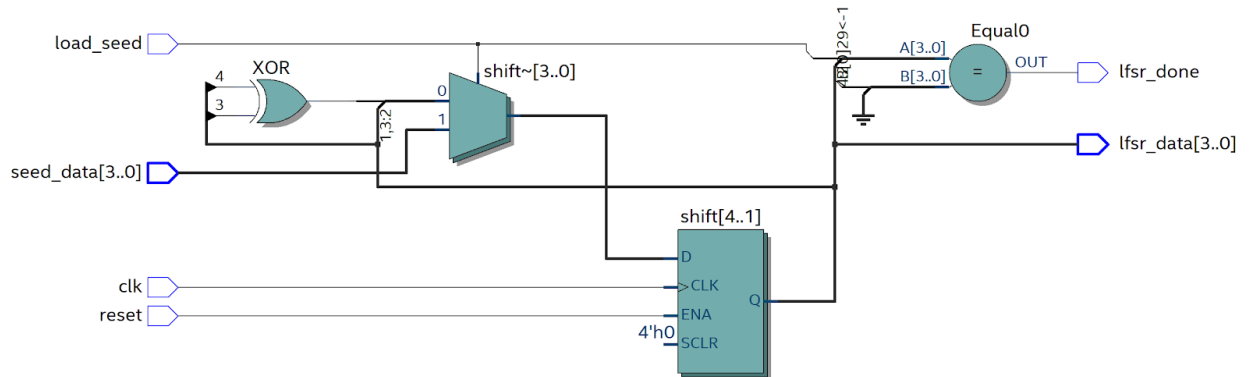


4. Post mapping schematic for N=4

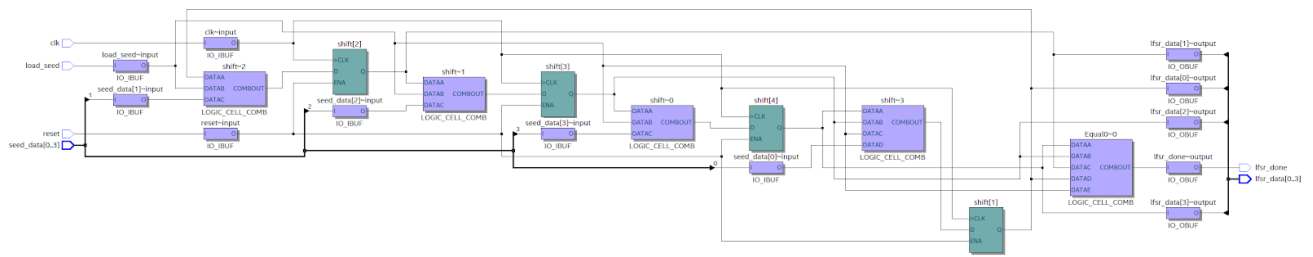


5. Post fitting schematic for N=4

 

6. Waveform simulation for N=4

 

Closer analysis of waveform

 

We can see that the pattern repeats every 15 cycles as stated by the polynomial equation $\text{period} = 2^N - 1 = 2^4 - 1 = 15$ cycles.

7. Transcript for N=4

```
# -- Compiling module lfsr_testbench
#
# Top level modules:
#   lfsr_testbench
# End time: 21:36:38 on Feb 10,2021, Elapsed time: 0:00:00
# Errors: 0, Warnings: 0
ModelSim> vsim work.lfsr_testbench
# vsim work.lfsr_testbench
# Start time: 21:36:46 on Feb 10,2021
# Loading sv_std.std
# Loading work.lfsr_testbench
# Loading work.lfsr
```


```

# time=11410, reset=1 clk=1 load_seed=0 count= 7
# time=11420, reset=1 clk=0 load_seed=0 count= 7
# time=11430, reset=1 clk=1 load_seed=0 count=15
# time=11440, reset=1 clk=0 load_seed=0 count=15
# time=11450, reset=1 clk=1 load_seed=0 count=14
# time=11460, reset=1 clk=0 load_seed=0 count=14
# time=11470, reset=1 clk=1 load_seed=0 count=12
# time=11480, reset=1 clk=0 load_seed=0 count=12
# time=11490, reset=1 clk=1 load_seed=0 count= 8
# time=11500, reset=1 clk=0 load_seed=0 count= 8
# time=11510, reset=1 clk=1 load_seed=0 count= 1
# time=11520, reset=1 clk=0 load_seed=0 count= 1
# time=11530, reset=1 clk=1 load_seed=0 count= 2
# time=11540, reset=1 clk=0 load_seed=0 count= 2
# time=11550, reset=1 clk=1 load_seed=0 count= 4
# time=11560, reset=1 clk=0 load_seed=0 count= 4
# time=11570, reset=1 clk=1 load_seed=0 count= 9
# time=11580, reset=1 clk=0 load_seed=0 count= 9
# time=11590, reset=1 clk=1 load_seed=0 count= 3
# time=11600, reset=1 clk=0 load_seed=0 count= 3
# time=11610, reset=1 clk=1 load_seed=0 count= 6
# time=11620, reset=1 clk=0 load_seed=0 count= 6
# time=11630, reset=1 clk=1 load_seed=0 count=13
# time=11640, reset=1 clk=0 load_seed=0 count=13
# time=11650, reset=1 clk=1 load_seed=0 count=10
# time=11660, reset=1 clk=0 load_seed=0 count=10
# time=11670, reset=1 clk=1 load_seed=0 count= 5
# time=11680, reset=1 clk=0 load_seed=0 count= 5
# time=11690, reset=1 clk=1 load_seed=0 count=11
# time=11700, reset=1 clk=0 load_seed=0 count=11
# time=11710, reset=1 clk=1 load_seed=0 count= 7
# time=11720, reset=1 clk=0 load_seed=0 count= 7
# time=11730, reset=1 clk=1 load_seed=0 count=15
# time=11740, reset=1 clk=0 load_seed=0 count=15
# time=11750, reset=1 clk=1 load_seed=0 count=14
# time=11760, reset=1 clk=0 load_seed=0 count=14

```


LFSR analysis:

 For $N=4$, the LFSR has 4 shift registers with a XOR gate that receives the most left (FF4) and second to most (FF3) values as inputs, while this XOR's output is fed into the rightmost shift register (FF1) as the bits continue to shift left. The truth table for the XOR gate is shown below:




a	b	$a \oplus b$
0	0	0
0	1	1
1	0	1
1	1	0

 
The truth table explains the output lfsr_data from the simulation as shown in the diagram below:




\Rightarrow lfsr_data = 1110

 

\Rightarrow lfsr_data = 1100

 


\Rightarrow lfsr_data = 1000

 

\Rightarrow lfsr_data = 0001


... so on

8. Waveform simulation of N=2

 


Repeats every **Period** = $2^N - 1 = 2^2 - 1 = 3$ cycles


Diagram to explain how the bits are shifted and changed due to the XOR.

 

\Rightarrow lfsr_data = 10

 


\Rightarrow lfsr_data = 01

 


\Rightarrow lfsr_data = 11

9. Waveform simulation for N=3

 


Repeats every **Period** = $2^N - 1 = 2^3 - 1 = 7$ cycles


Diagram to explain how the bits are shifted and changed due to the XOR.

 

\Rightarrow lfsr_data = 110

 

\Rightarrow lfsr_data = 100

 

\Rightarrow lfsr_data = 001

. . . so on