

## johnson\_counter:

### 1. Testbench

```
1  `timescale 1ns/1ns
2  //Johnson Counter Testbench Code
3  module johnson_counter_testbench;
4      logic clock, reset, preset;
5      logic[3:0] load_cnt, count;
6
7      // Instantiate design under test
8      johnson_counter design_instance(
9          .clk(clock),
10         .clear(reset),
11         .preset(preset),
12         .load_cnt(load_cnt),
13         .count(count)
14     );
15
16     initial begin
17         // Initialize Inputs
18         reset = 0;
19         preset = 1;
20         clock = 0;
21         load_cnt = 4'b0000;
22
23         // Wait 10 ns for global reset to finish and start counter
24         #10;
25         reset = 1;
26
27         #10;
28         preset = 0;
29         load_cnt = 4'b0000;
30
31         #20;
32         preset = 1;
33
34         // Wait for 200ns and reset counter
35         #340ns;
36         reset=0;
37
38         // Wait for 20ns and start counter again
39         #20ns;
40         reset=1;
41
42         #10;
43         preset = 0;
44         load_cnt = 4'b1000;
45
46         #10;
47         preset = 1;
48
49         // Wait for 10ns
50         #100ns;
51
52         // terminate simulation
53         $finish();
54     end
55
56     // Clock generator logic
57     always@(clock) begin
58         #10ns clock <= !clock;
59     end
60
61     // Print input and output signals
62     initial begin
63         $monitor(" time=%0t,  clear=%b  clk=%b  count=%d", $time, reset, clock, count);
64     end
65
66 endmodule
```

## 2. RTL model


```

1 module johnson_counter (
2     input logic clk, clear, preset,
3     input logic [3:0] load_cnt,
4     output logic [3:0] count
5 );
6
7 always @(posedge clk or negedge clear) begin
8     if (!clear) count <= 4'b0000;
9     else if (!preset) count <= load_cnt;
10    else begin
11        count <= count >> 1;
12        count[3] <= ~count[0];
13    end
14 end
15 endmodule: johnson_counter


```

The 4 bits johnson\_counter code is very similar to that of the ring counter code, the only change is that the inverse of the output of the final shift register is fed as the input of the first shift register. Compared to the ring counter code, the only change in the johnson\_counter code is the addition of the negation operator to inverse count[0]; count[3]<=~count[0].

### 3. RTL schematic

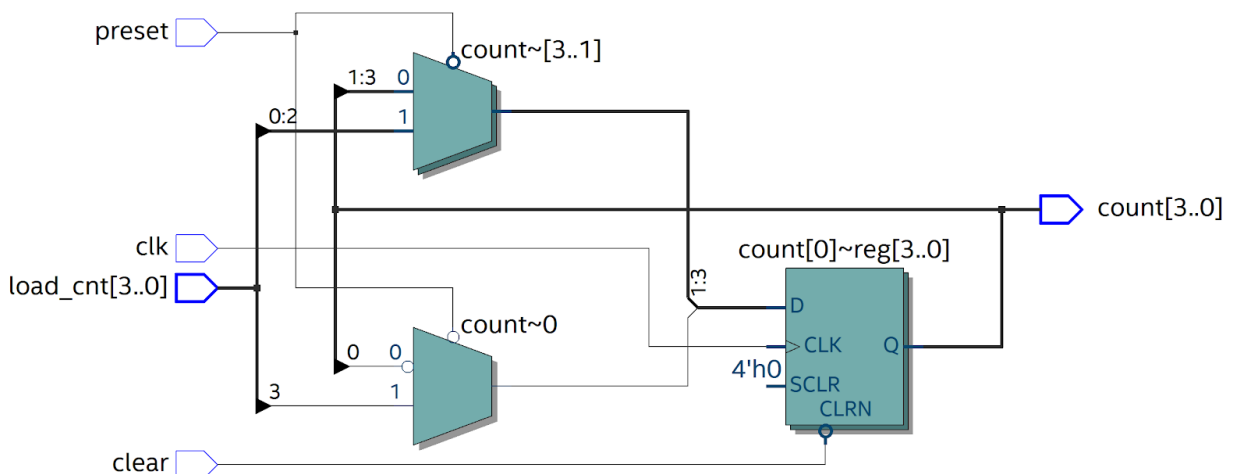


#### 4. Post mapping schematic

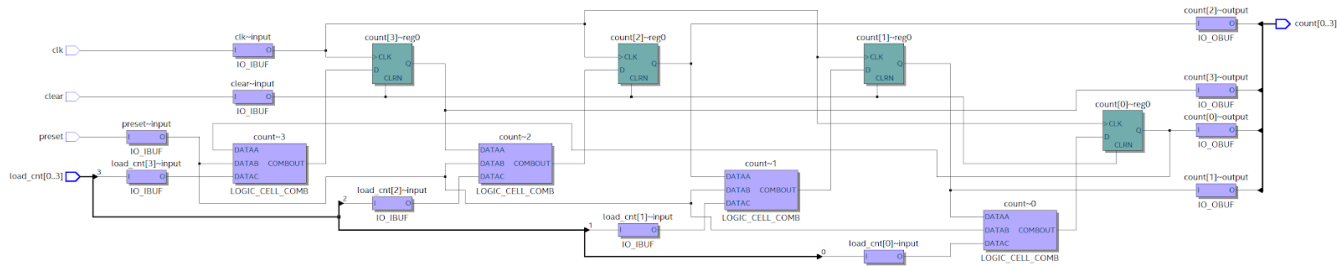

There are 4 ALUT since there are 4 shift registers, each ALUT has 3 inputs: preset, load\_cnt[0:3], and shift register output Q. The output of ALUT count~0, COMBOUT, is the input of shift register count[0], but the output of this register feeds into the input DATAA of ALUT count~3. This feedback behavior creates an 8 bit pattern (2N) that repeats every 8 clock cycles.

#### 5. Post fitting schematic

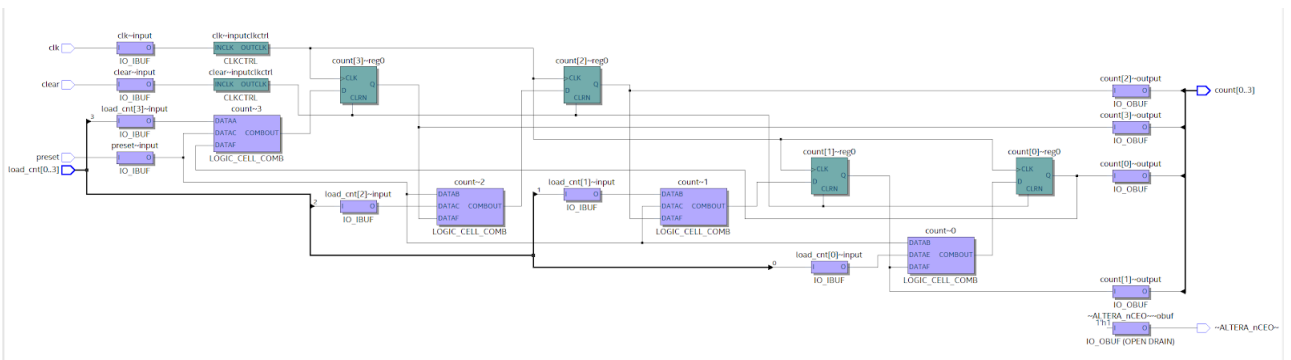


## 6. Resource Usage table

	Resource	Usage
1	Estimated ALUTs Used	4
1	-- Combinational ALUTs	4
2	-- Memory ALUTs	0
3	-- LUT_REGS	0
2	Dedicated logic registers	4
3		
4	Estimated ALUTs Unavailable	0
1	-- Due to unpartnered combinational logic	0
2	-- Due to Memory ALUTs	0
5		
6	Total combinational functions	4
7	Combinational ALUT usage by number of inputs	
1	-- 7 input functions	0
2	-- 6 input functions	0
3	-- 5 input functions	0
4	-- 4 input functions	0
5	-- <=3 input functions	4
8		
9	Combinational ALUTs by mode	
1	-- normal mode	4
2	-- extended LUT mode	0
3	-- arithmetic mode	0
4	-- shared arithmetic mode	0
10		
11	Estimated ALUT/register pairs used	4
12		
13	Total registers	4
1	-- Dedicated logic registers	4
2	-- I/O registers	0
3	-- LUT_REGS	0
14		
15		
16	I/O pins	11
17		
18	DSP block 18-bit elements	0
19		
20	Maximum fan-out node	preset~input
21	Maximum fan-out	4
22	Total fan-out	39
23	Average fan-out	1.30

Number of ALUT: 4 (11 I/O pins)

Number of functions: 4 (3 input functions)

## 7. Simulation

 

The johnson\_counter repeats a pattern every 8 clock cycles, the pattern goes 1000, 1100, 1110, 1111, 0111, 0011, 0001, 0000; then it repeats. The counter passes the 4 logic blocks 0, then to 4 logic block 1, shifting left each time. This in turn creates a pattern the repeats every 8 clock cycles since each passed block (0 and 1) takes 4 cycles.

```

Transcript
#
# Top level modules:
#   johnson_counter_testbench
# End time: 22:56:38 on Feb 01,2021, Elapsed time: 0:00:00
# Errors: 0, Warnings: 0
ModelSim> vsim work.johnson_counter_testbench
# vsim work.johnson_counter_testbench
# Start time: 22:56:43 on Feb 01,2021
# Loading sv_std.std
# Loading work.johnson_counter_testbench
# Loading work.johnson_counter
add wave -position insertpoint sim:/johnson_counter_testbench/*
VSIM6> run -all
# time=0,   clear=0   clk=0   count= 0
# time=10,  clear=1   clk=1   count= 8
# time=20,  clear=1   clk=0   count= 8
# time=30,  clear=1   clk=1   count= 0
# time=40,  clear=1   clk=0   count= 0
# time=50,  clear=1   clk=1   count= 8
# time=60,  clear=1   clk=0   count= 8
# time=70,  clear=1   clk=1   count=12
# time=80,  clear=1   clk=0   count=12
# time=90,  clear=1   clk=1   count=14
# time=100, clear=1   clk=0   count=14
# time=110, clear=1   clk=1   count=15
# time=120, clear=1   clk=0   count=15
# time=130, clear=1   clk=1   count= 7
# time=140, clear=1   clk=0   count= 7
# time=150, clear=1   clk=1   count= 3
# time=160, clear=1   clk=0   count= 3
# time=170, clear=1   clk=1   count= 1
# time=180, clear=1   clk=0   count= 1
# time=190, clear=1   clk=1   count= 0
# time=200, clear=1   clk=0   count= 0
# time=210, clear=1   clk=1   count= 8
# time=220, clear=1   clk=0   count= 8

```

